

ELEC 344 - 201: Applied Electronics and Electromechanics

Instructor: Ignacio Galiano Zurbriggen

TAs: Daniel Hsu, Abbas Arshadi, Matthieu Amyotte, Jorge May

Tutorial 3

1) Using the circuit in Fig. 1:

- Plot all the relevant waveforms (V_{out} , v_a , v_b , v_c , i_a , i_b , i_c).
- What is the output voltage? And the current?

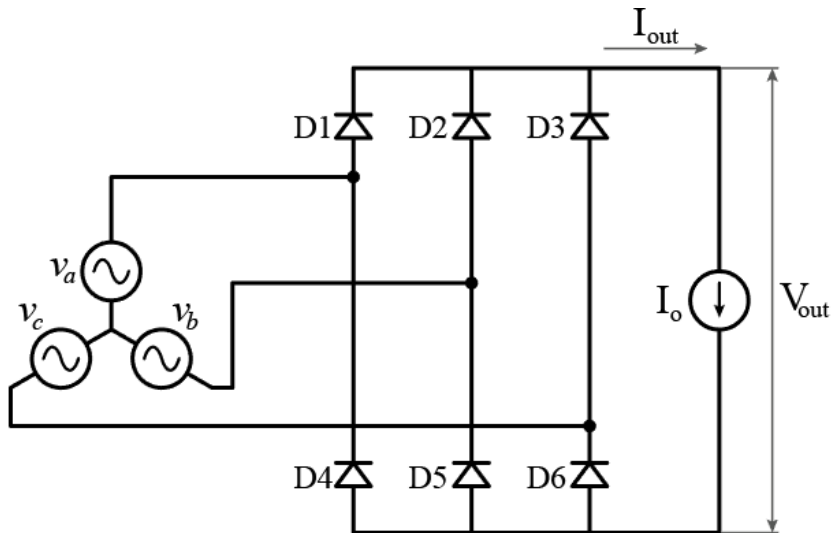


Figure 1 – Three Phase Rectifier

2) Figure 2 illustrates a buck converter

- Calculate the duty cycle for an output voltage of 10 V.
- Plot all relevant waveforms with their values (v_L , i_L , i_C).
- What happens if the switching frequency is increased to 100 kHz.

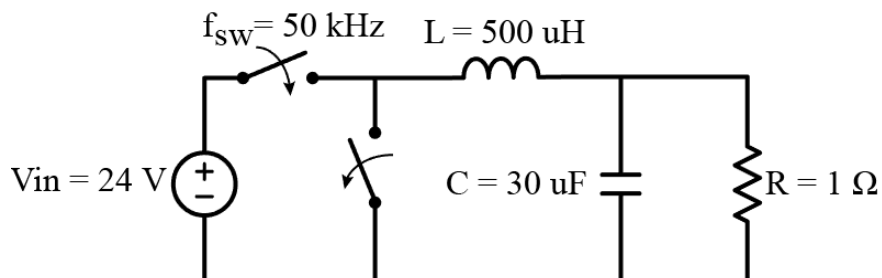


Figure 2 – Buck Converter

- 3) For the Operational Amplifier configurations shown in Fig 3, 4 and 5 derive the relationship output/input for each case.

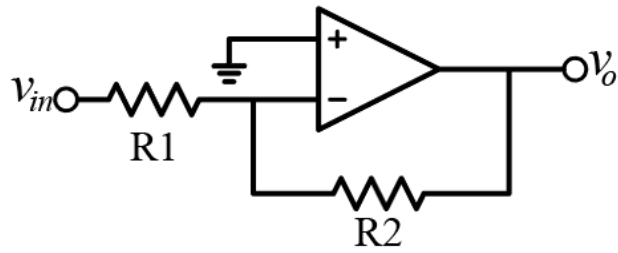


Figure 3 - Inverting

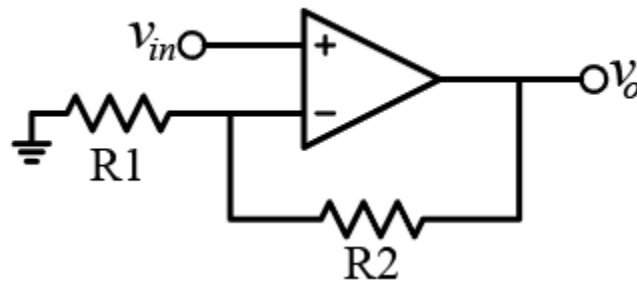


Figure 4 - Non inverting

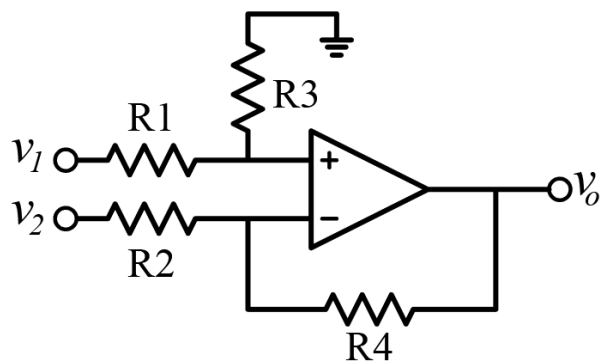


Figure 5 - Differential