

ELEC 344 - 201: Applied Electronics and Electromechanics

Instructor: Ignacio Galiano Zurbriggen

TAs: Daniel Hsu, Abbas Arshadi, Matthieu Amyotte, Jorge May

Tutorial 5

1). Consider a permanent-magnet dc motor with the following parameters:

- winding resistance, $R_a : 0.35 \, \Omega$
- winding inductance, $L_a : 1.5 \, \text{mH}$
- motor voltage constant, $k_E : 0.5 \, \text{V}/(\text{rad/s})$
- motor torque constant, $k_T : 0.5 \, \text{Nm/A}$
- total effective inertia, $J_m : 0.02 \, \text{kg}\cdot\text{m}^2$

The rated torque of this motor is 4 Nm. Plot the steady state torque-speed characteristics for the armature voltage, $V_a = 100 \, \text{V}$, 60 V, and 30 V.

2). The motor in Problem 1 is driving a load whose torque requirement remains constant at 3 Nm, independent of speed. Calculate the armature voltage V_a to be applied in steady state, if this load is to be driven at 1500 rpm.

3). The motor in Problem 1 is supplied by a switch-mode dc-dc converter that has a dc-bus voltage $V_d = 200 \, \text{V}$. The switching frequency $f_s = 25 \, \text{kHz}$. Calculate and plot the waveforms for $v_a(t)$, e_a , $i_a(t)$, $i_d(t)$, and $T_{em}(t)$, under the following conditions:

(a) Motoring in forward direction at 1500 rpm, supplying a load of 3 Nm.

(b) Regenerative braking from conditions in (a), with a current of 10 A. (Assume that the inertia is large, and thus the speed changes very slowly.)

4). Assume that the dc-motor of Problem 1 has a wound field. The rated speed is 2000 rpm. Assume that the motor parameters are somehow kept the same as in Problem 1 with the rated field current of 1.5 A. As a function of speed, show the capability curve by plotting the torque and the field current i_f , if the speed is increased up to twice its rated value.