


# ELEC 344 - 201: Applied Electronics and Electromechanics

**Instructor:** Ignacio Galiano Zurbriggen

**TAs:** Daniel Hsu, Abbas Arshadi, Matthieu Amyotte, Jorge May

## Tutorial 2

- 1) In the circuit shown in Fig. 1, the input voltage is given by:  $v_{in} = 110V \sin(\omega t)$ , assuming that the frequency is 60 Hz.
  - a) Find the input current  $i_{in}$  (amplitude and phase)
  - b) Find the time delay and the phase shift of the current vs. voltage waveform.
  - c) Calculate the power factor. Is this a good power factor? How can we improve it?

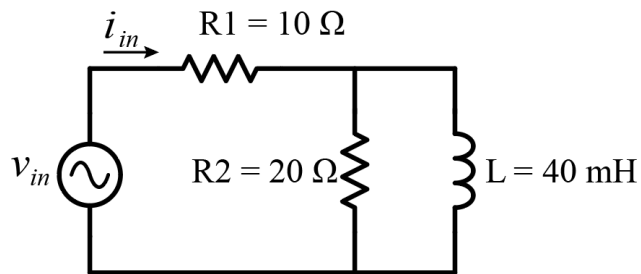

**Figure 1 – AC circuit**

- 2) A **100 $\mu$ F** capacitor is added in parallel with the resistor and inductor:
  - a) Calculate the new current amplitude and phase.
  - b) Find the time delay and the phase shift of the current vs.. voltage waveform.
  - c) Calculate the power factor and compare it with the one obtained in 1)

- 3) Y-Connected 3-phase load. Prove that for the case of a balanced 3-phase source and a balanced 3-phase load, the load center point  $V_N = 0$ .

HINT: use the superposition theorem.

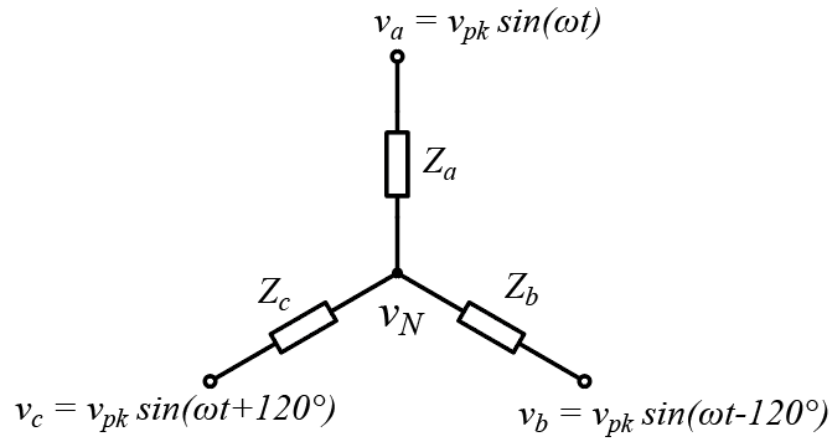


Figure 2 – 3-Phase AC Circuit

- 4) Derive the RMS of a periodic, symmetrical square and triangular wave, respectively (given that the amplitude is  $V_{pk}$ .)