

# ELEC 344 Lab Report 4

Kelvin Hsu 46308152  
Alex Lim 47049151  
Matthew Chan 52416154

April 10, 2019

## 5A-1)

$R_1$  and  $L_m$  can be found using the no load test where  $S \sim 0$  and rotor circuit can be treated as open circuit.

### Calculating $R_1$

$$P_{nl} = I_{rms} V_{rms} \cos(\theta)$$

$$R_1 = \frac{P_{nl}}{I_{rms}^2} / 2 = 0.345 / 2 = 0.1725 \Omega$$

### Calculating $L_m$

Assuming  $L_m \gg L_{l1}$ .

$$P(\text{Reactive Power}) = \sqrt{I_{rms}^2 V_{rms}^2 - P_{nl}^2} = \omega * L_{l1} * I_{rms}^2$$

$$\omega = 2\pi 60 \text{ Hz}$$

$$L_{lm} = 0.0086529 \text{ H}$$

### Calculating $L_{l1}$ , $L_{l2}$ , and $R_2$

$L_{l1}$ ,  $L_{l2}$ , and  $R_2$  can be found using block motor test. Assuming the impedance of  $L_{l2}$  in series with  $R_2$  is much smaller than the impedance of  $L_m$ .

$$R_2 = \frac{P_{total}/3}{I_{rms}^2} = 0.2839 \Omega$$

$$(L_{l1} + L_{l2}) \omega I_{rms}^2 = \sqrt{(V_{rms}^2 I_{rms}^2) - (P_{total}/3)^2}$$

$$L_{l1} = L_{l2} = 0.000731913 \text{ H}$$

### Calculating Number of Poles

$$\text{motor rpm} = \frac{120 f_{in}}{p}$$

$$p = 120 * 60 / 1750 = 4.11 \sim 4$$

## Calculating Power Factor

$$\omega_{synchronous} = 0.5 * 2 * \pi * 60 = 188.495rad/s$$

$$\omega_{rotor} = 1750rpm * 2\pi/60 = 183.259rad/s$$

$$\omega_{slip} = 5.23598rad/s$$

$$\theta = \tan^{-1}\left(\frac{\omega_{slip}L_{l2}}{R_2}\right) = 0.77335^\circ$$

$$\cos(\theta) = 0.9999$$

## 5A-2

From Table-6,  $R_2$  is estimated. Looking at the table, the first and the 4th measurements are outliers. The 2nd and 3rd give the best estimate of  $R_2$  because the slip is smaller relative to the later measurements. The estimate is also really close to the resistance calculated in 5A-1.

$$R_2 = 0.32\Omega$$

## 5B:Equivalent Circuit vs Measured Comparison

From the equivalent circuit, we found the Thevenin Equivalent treating the rotor circuit as load such that rotor current can be found.

Python script is used to calculate the Thevenin equivalent parameters.

$$V_{th} = 17.95788$$



$$Z_{th} = 0.14699 + 0.262784j$$

$$I_{rotor} = V_{th}/Z_{total}$$

$$Z_{total} = 0.14669 + R_{rotor}/s + (0.262784 + X_{l2})j$$

$$P_{em} = 3 * I_{rotor}^2 * R_{rotor} * (1 - s)/s$$

$$T_{em} = P_{em}/\omega_{rotor}$$

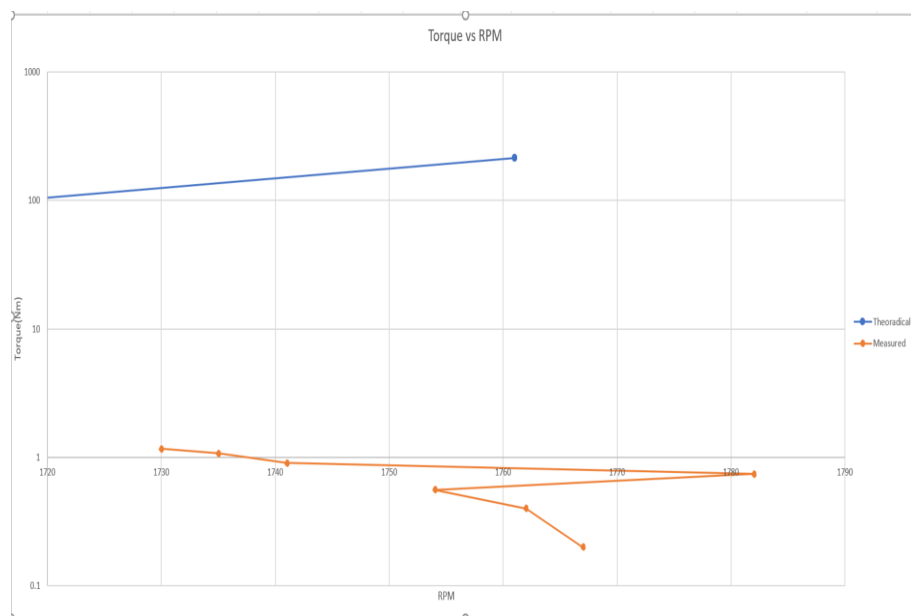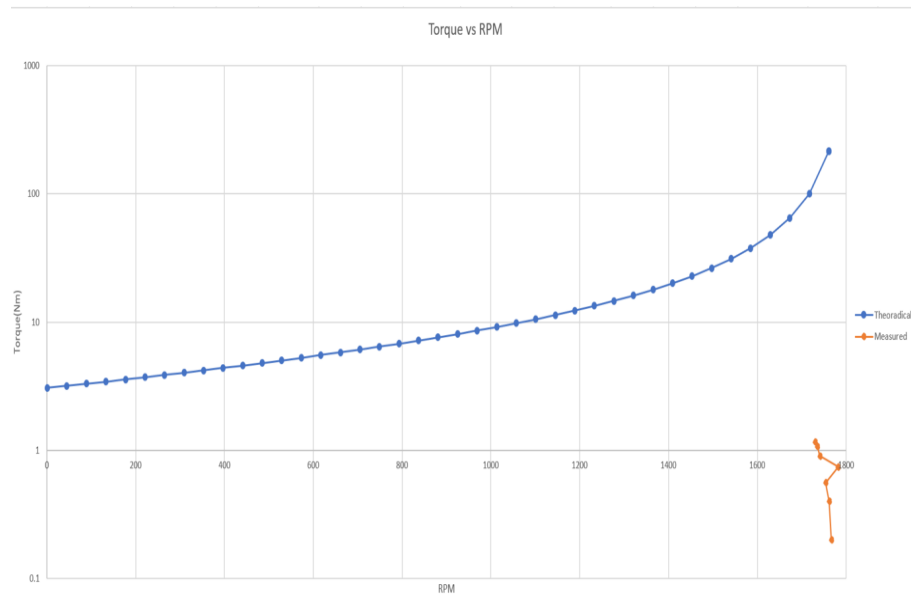

As shown in the graphs, the measured values starts to decrease just before the theoretical reaches the pull out torque and start decreasing. Ideally both graph should reach 0 torque at 1800 rpm since  $s$  will approach 0.